

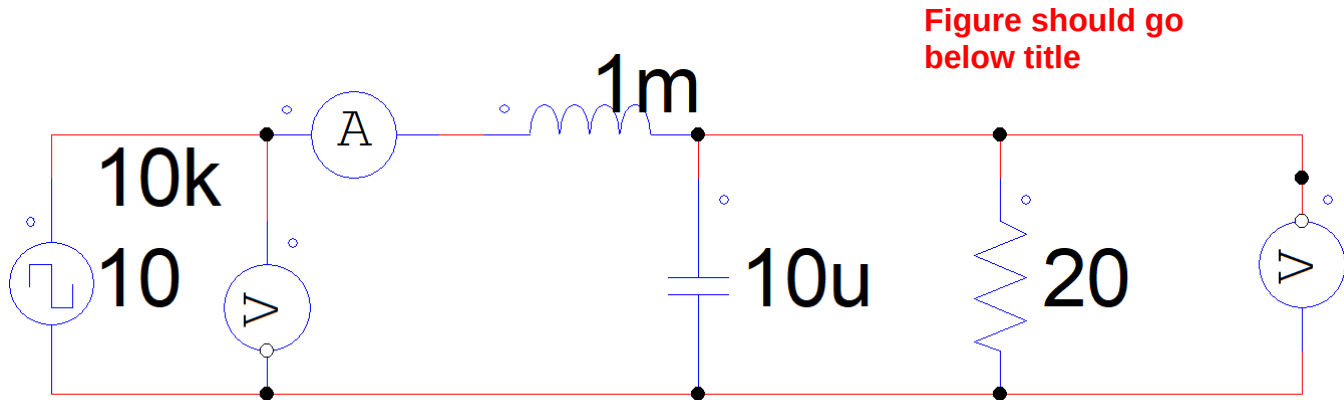


Fig. 1. PSIM schematic of the circuit: square-wave source (10 kHz), 1 mH inductor, 10 μ F capacitor and 20 Ω resistor, with voltage probes v_i and v_o and inductor current probe i_L .

ELEC 451 Power Electronics

Lab 0: Introduction to Simulations and Experimental Instruments

Student Name 1, 00000000, Student Name 2, 00000000, Student Name 3, 00000000

I. INTRODUCTION

THIS is Lab 0 of ELEC 451. Its principal focus is on the basics of PSIM, the proper use and calibration of the measurement probes used in the lab (passive, differential and current probes), and performing mathematics such as the Fast Fourier Transform (FFT) in both PSIM and on the oscilloscope. Delete, unnecessary imo

Successful completion and understanding of the lab allows the team to progress through the rest of the labs while spending minimal time on learning the basics of the equipment.

The overarching scientific objective of this lab, in addition to the practical skills, is to demonstrate how simulation and real-world results differ or overlap.

This report is organized as follows. Section II presents the PSIM simulations: circuit setup, transient and steady-state waveforms, the effect of the time step, mean-value measurements and the FFT. Section III describes the experimental work with the oscilloscope: probe calibration, time-domain measurements and the FFT. Section IV concludes the report.

The diagram is missing the i_L and v_i labels.

II. SIMULATION

"Section IV is a summary and conclusion of our findings."

A. Circuit Setup (Activity 1)

The circuit in Fig. 1 was built in PSIM. A 10 kHz square-wave voltage source feeds a 1 mH inductor in series, followed by a 10 μ F capacitor in parallel with a 20 Ω resistor. The source voltage v_i , the output voltage v_o and the inductor current i_L are measured with probes placed according to the polarity shown.

B. Waveform Captures (Activities 2 and 3)

Fig. 2 shows v_i , v_o and i_L over the first 5.5 ms as first captured. The square-wave source correctly swings between 0 V and 10 V, as specified in Table ??; v_o overshoots to about 7.3 V before settling to a steady-state ripple around 5 V.

The Simulation Control tool was then added, with a time step of 1 μ s and a total time of 2 ms, so that the complete transient of the signals is visible (Fig. 3); the signals reach steady state after roughly 1 ms. Fig. 4 zooms in to five cycles of the steady-state waveforms.

C. Time Step (Activity 4)

The waveforms were captured for a large time step (1×10^{-5} s, Fig. 5), a reasonable time step (1 μ s, Fig. 6) and a very small time step (1×10^{-7} s, Fig. 7). Even at this scale, the waveforms remain clean, since 20 Ω load strongly damps the ringing regardless of step size; a closer, few-cycle zoom would be needed to see any edge distortion at the largest step.

The more time steps taken, the longer the software takes to process the simulation. A smaller time step also helps to avoid aliasing and clipping of the signal.

We aren't taking the FFT in Act 4, so aliasing doesn't matter yet?

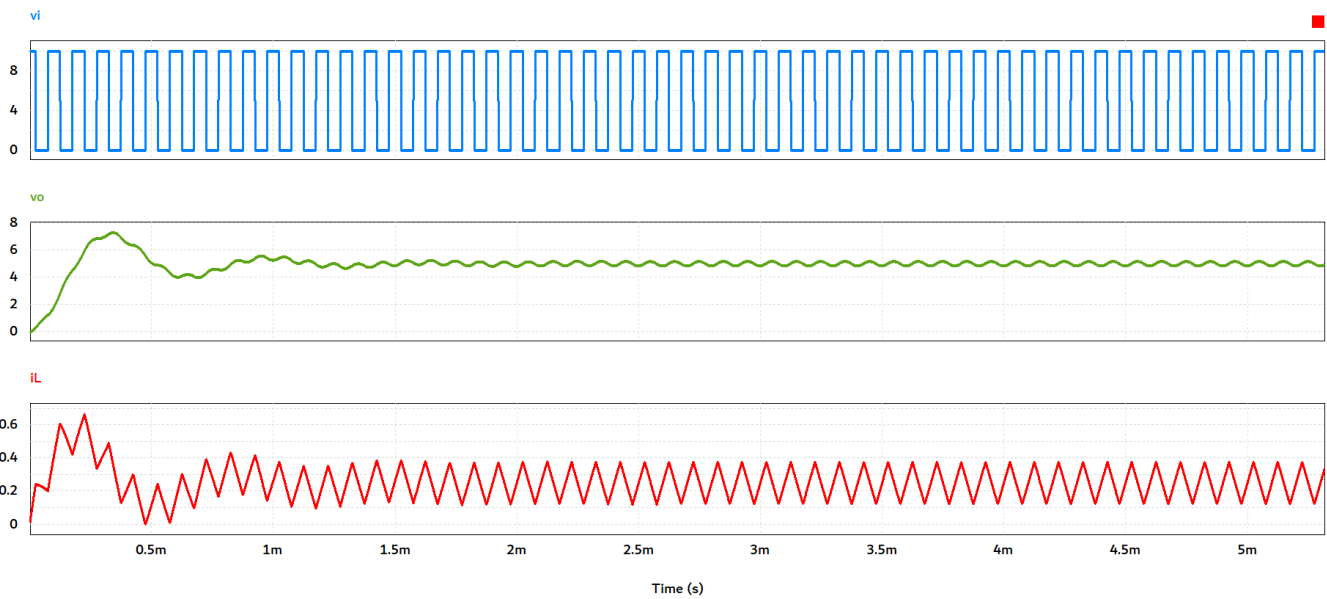


Fig. 2. Simulated waveforms v_i , v_o and i_L (top to bottom) as first captured.

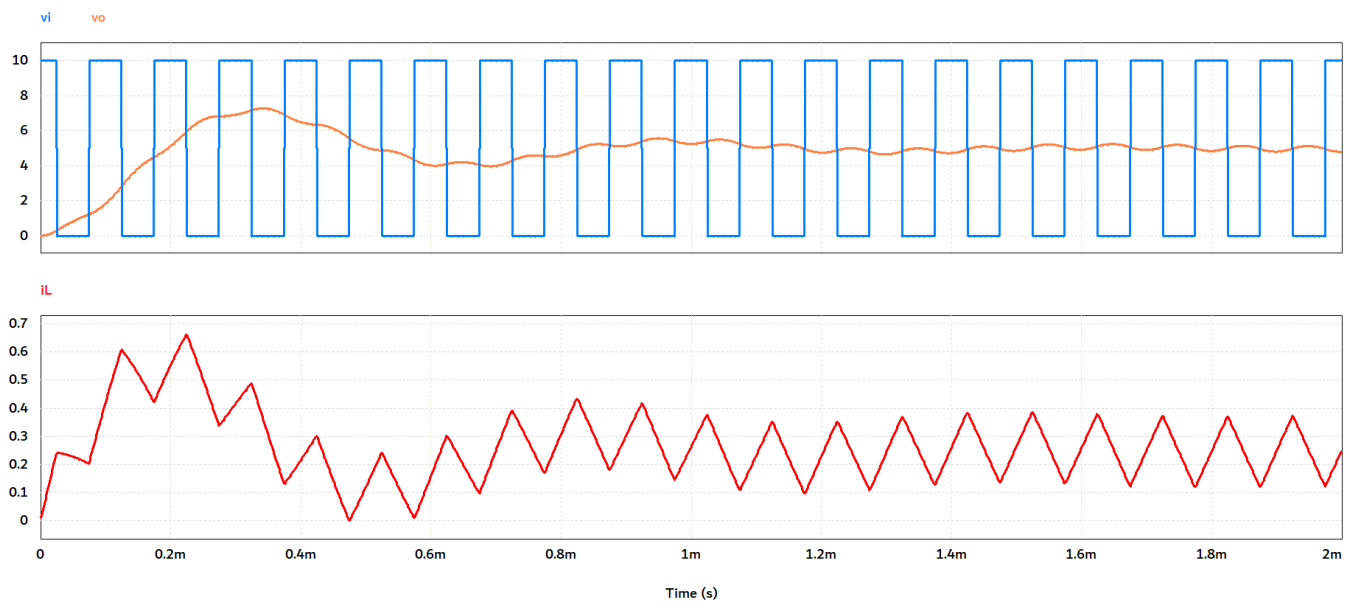


Fig. 3. Transient and steady-state waveforms with a 1 μ s time step and a total time of 2 ms: v_i and v_o overlaid (top), i_L (bottom).

TABLE I
MEAN VALUES OVER 10 STEADY-STATE CYCLES

Time span	v_o (V)	i_L (A)
10 cycles	5.007	0.2495

D. Measurements (Activity 5)

The mean value of v_o and i_L was measured with the Measure cursor tool over 10 complete steady-state cycles (1.00 ms). The results are listed in Table I.

Fig. 8 shows the corresponding Measure-tool captures for v_o and i_L .

It looks like we're missing 2 cycles, fraction of a third one, and several cycles (around 50) in Table I.

We also missed the discussion points 5b, 5c, 5d

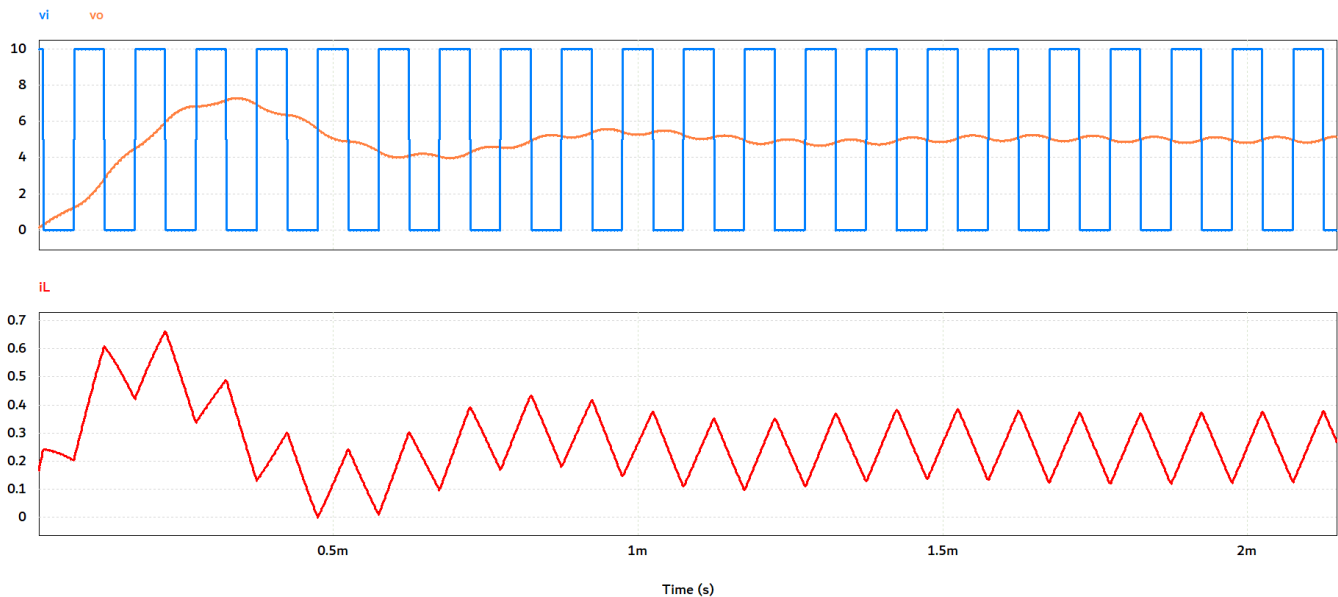


Fig. 4. Five cycles of the steady-state waveforms: v_i and v_o overlaid (top), i_L (bottom).

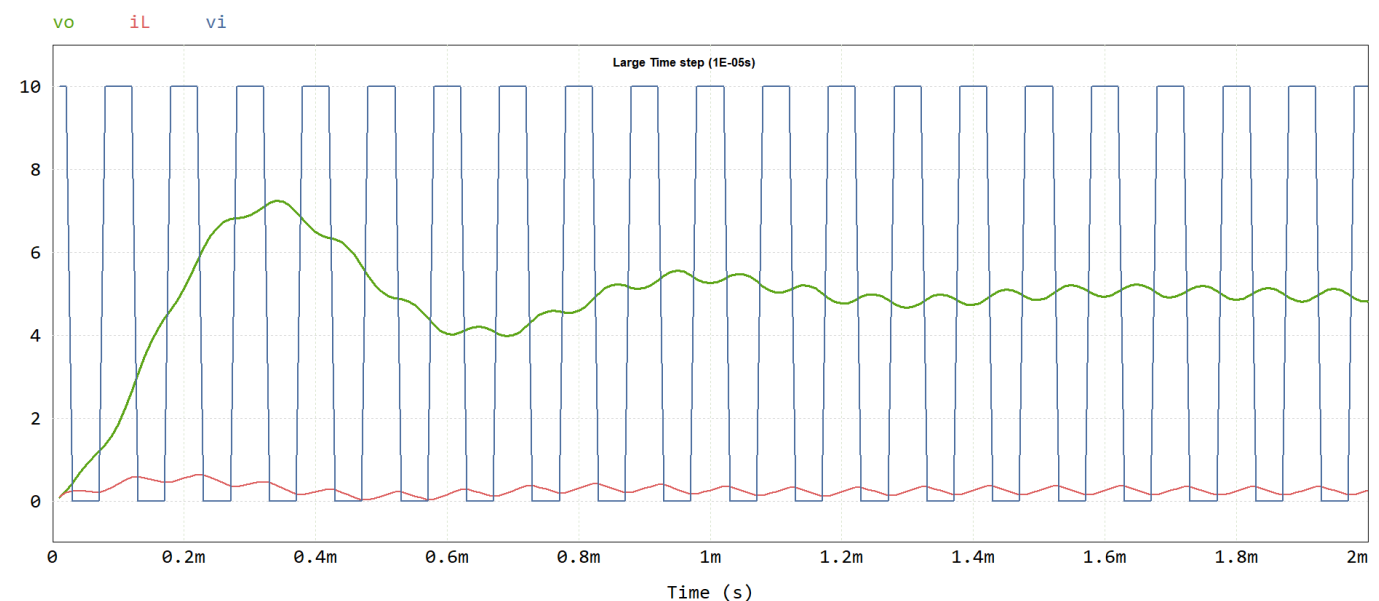


Fig. 5. Waveforms with a large time step (1×10^{-5} s): v_i , v_o and i_L overlaid.


E. FFT (Activity 6)

The triangular-wave voltage source (10 kHz, 1 V peak-to-peak, 2 V DC offset) was simulated and its FFT computed with Analysis/Perform FFT (Fig. 9); the fundamental appears clearly at 10 kHz.

The total simulation time was then reduced to below 10 cycles (Fig. 10(a)); the resulting FFT (Fig. 10(b)) shows a wider, less well-defined peak at 10 kHz because of the coarser frequency resolution. With the total time increased instead (Fig. 11), the fundamental at 10.0 kHz and the third harmonic at 30.1 kHz are both sharply resolved.

A longer total simulation time gives finer frequency resolution and a sharper, more legible FFT, while a short total time smears the peaks and makes the harmonics hard to see. This illustrates the Shannon–Nyquist trade-off encountered when varying the time step: enough samples are needed to resolve the spectrum clearly.

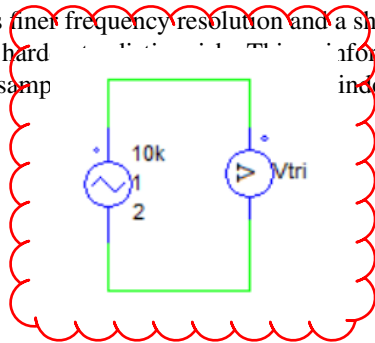Might be nice to include the circuit here



Also think we're missing discussion points from the lab report. Should be added in here.

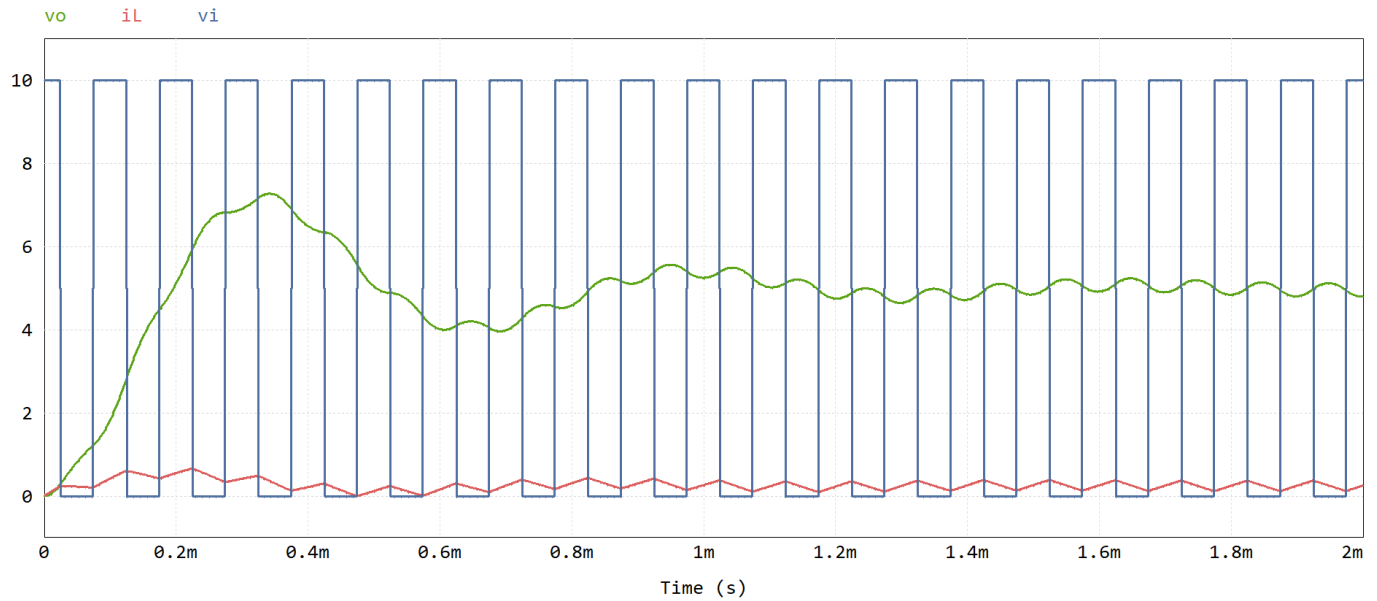
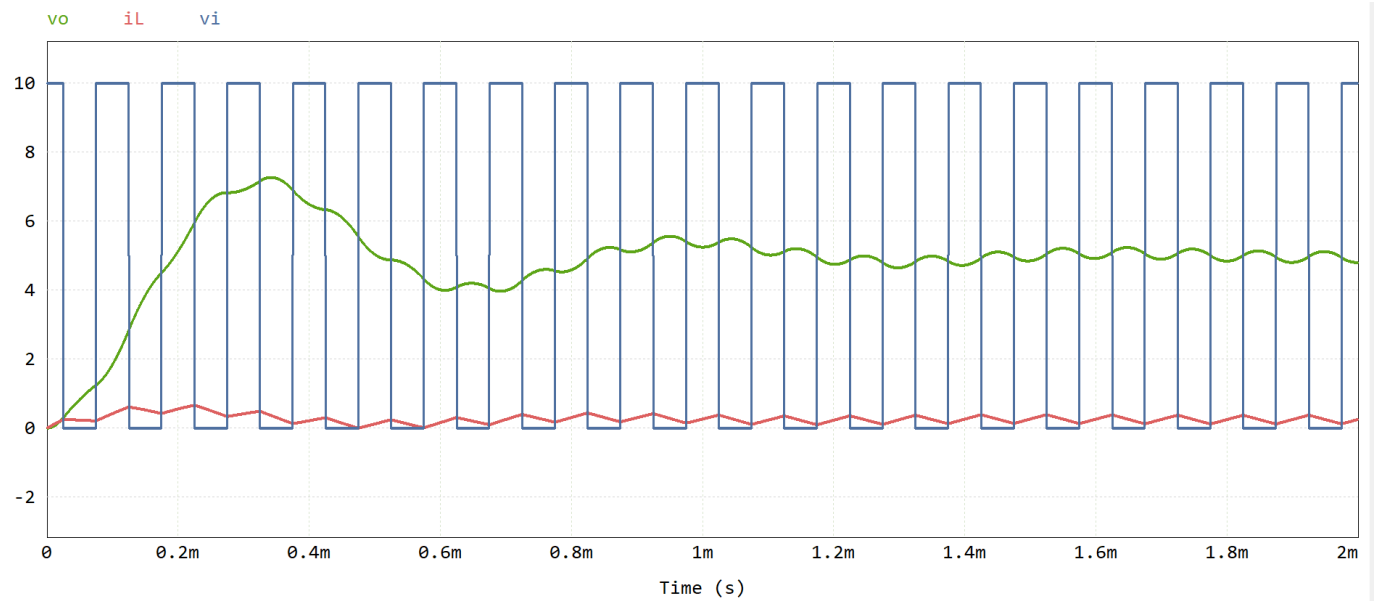
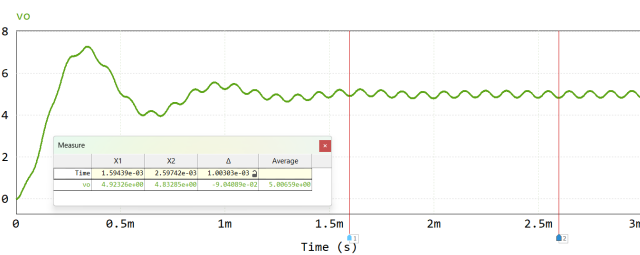
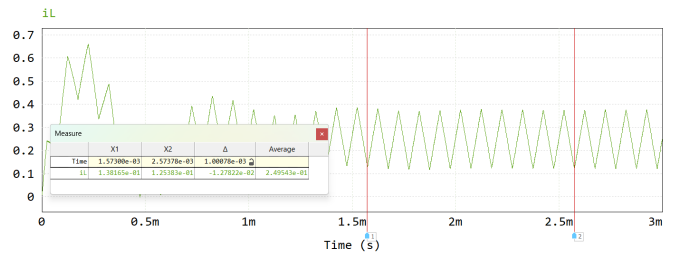
Fig. 6. Waveforms with a reasonable time step ($1 \mu\text{s}$): v_i , v_o and i_L overlaid.Fig. 7. Waveforms with a very small time step ($1 \times 10^{-7} \text{ s}$): v_i , v_o and i_L overlaid.(a) Output voltage v_o .(b) Inductor current i_L .

Fig. 8. Mean-value measurements over 10 steady-state cycles (1.00 ms).

A bit small, can we separate 8a and 8b?

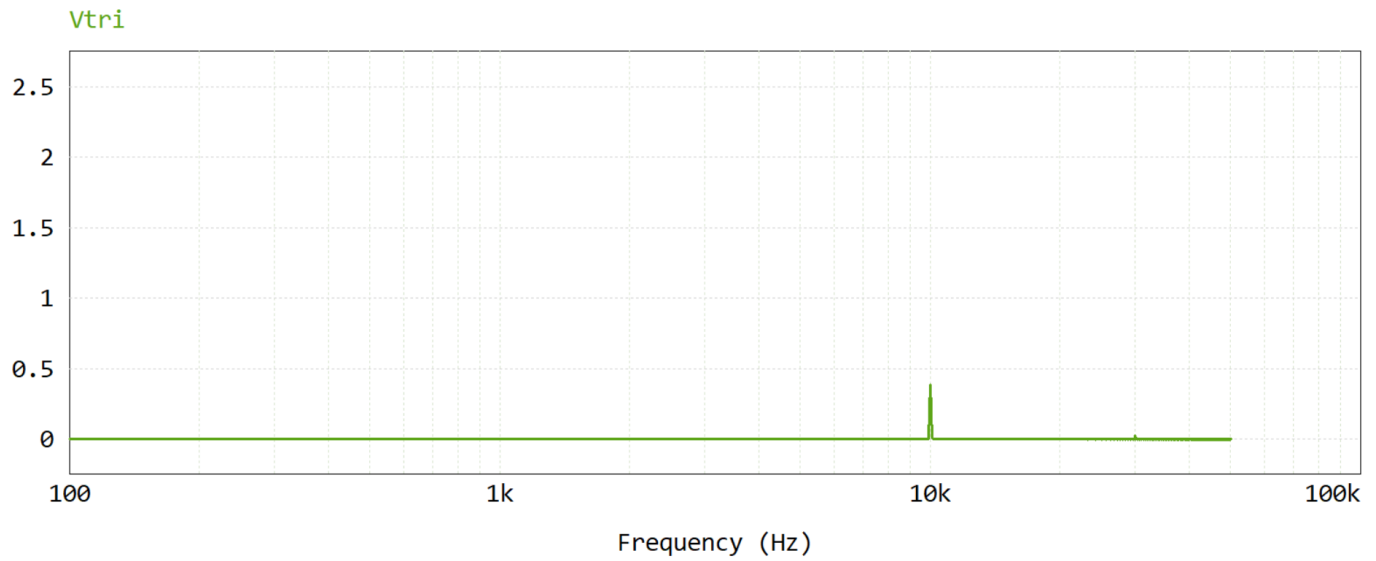


Fig. 9. FFT of the triangular-wave voltage, full span.

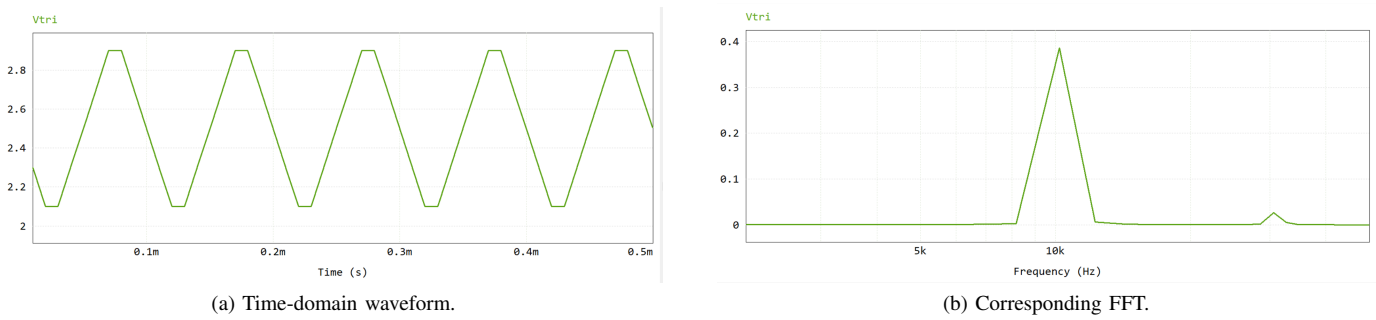


Fig. 10. Triangular-wave voltage with the total simulation time reduced to below 10 cycles.



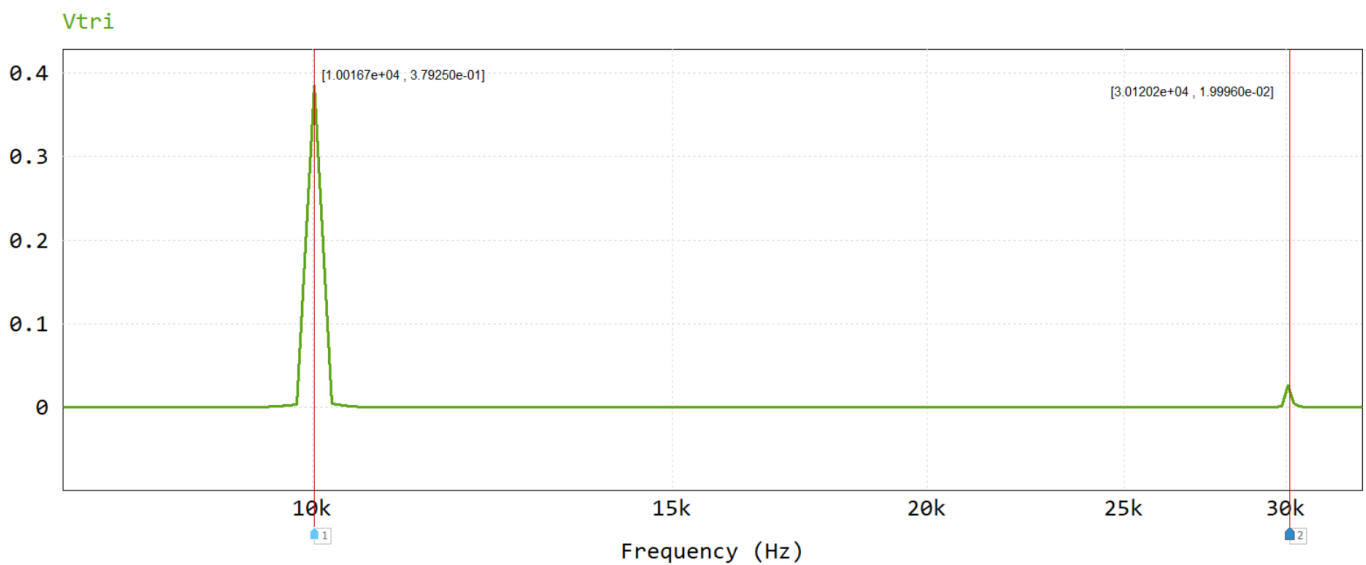


Fig. 11. FFT of the triangular-wave voltage with the total simulation time increased to more than 10 cycles. Cursors mark the fundamental (10.02 kHz, 0.379) and the third harmonic (30.12 kHz, 0.020).

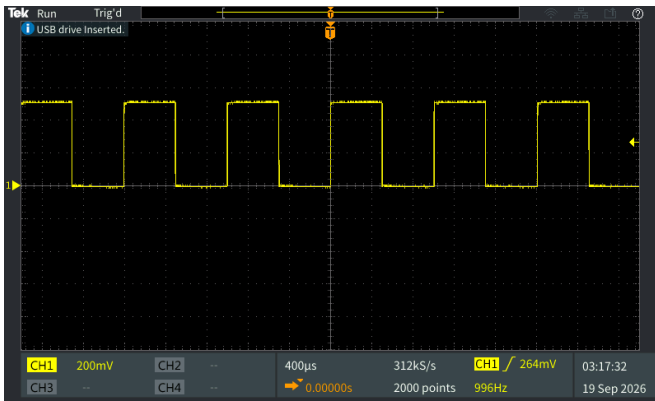


(a) Passive probe: clean test waveform.

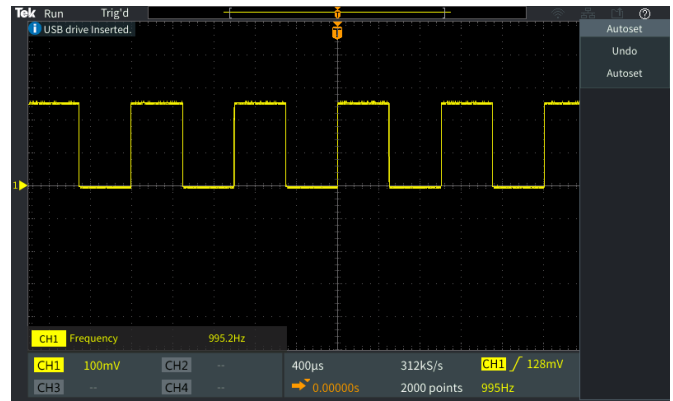


(b) Differential probe.

Fig. 12. Oscilloscope captures of the calibration signal.

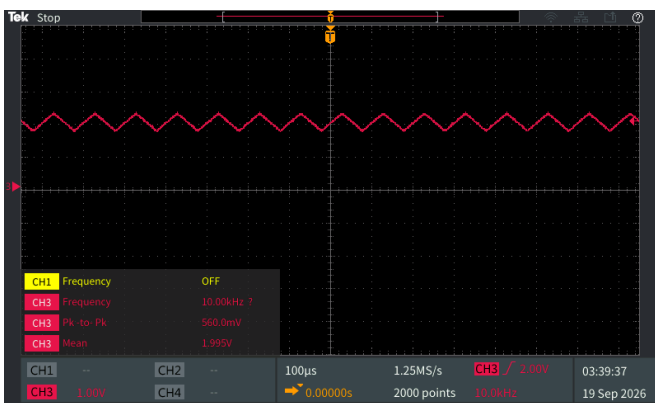

(a) 500 mV amplitude, 2 V offset.

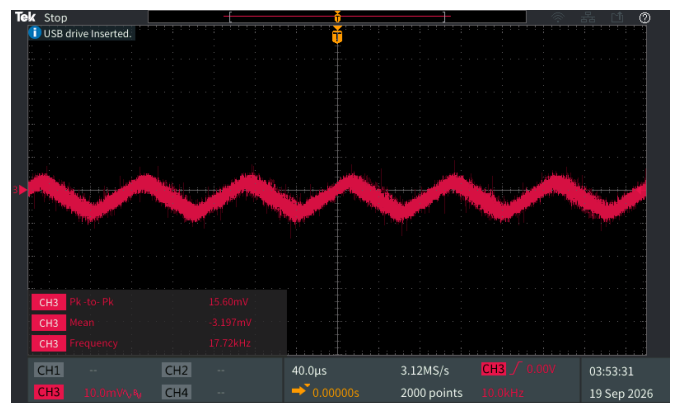

(b) 10 mV amplitude, 2 V offset, AC coupling.

Fig. 13. Oscilloscope captures of the 10 kHz triangular wave.

III. EXPERIMENT

A. Probe Calibration (Activity 1)

Before taking measurements, the probes were configured and calibrated against the calibration signal of the oscilloscope (a 1 kHz square wave) (Fig. 12).

B. Time-Domain Captures and Measurements (Activity 2)


A triangular wave (10 kHz, 500 mV amplitude, 2 V DC offset) from the function generator was displayed on the oscilloscope (Fig. 13(a)). The frequency and mean value measured by the scope (10.00 kHz and 1.995 V) match the generator settings, and the peak-to-peak amplitude read 560 mV for the 500 mV set on the generator.

When the amplitude was reduced to 10 mV, the details inside the signal became invisible because of noise. After changing the channel from DC to AC coupling and applying a high-frequency filter, the triangular shape could be recovered (Fig. 13(b)): the ripple came into view and, although the signal was still noisy, it could be analyzed and understood. The automatic measurements were nevertheless still affected by the noise, with 15.6 mV peak-to-peak and 17.72 kHz reported for a 10 mV, 10 kHz signal.

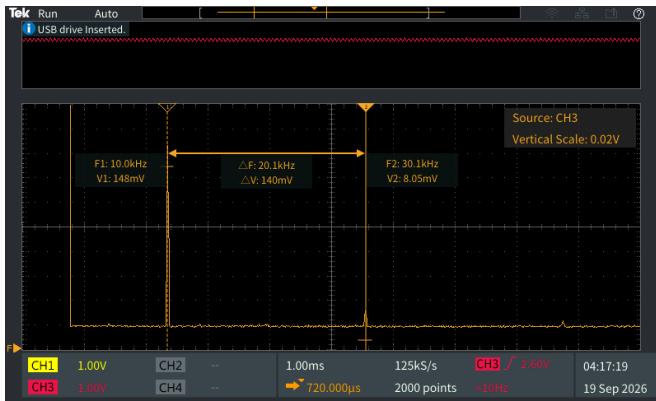C. Frequency-Domain Captures and Measurements (Activity 3)

The team expected the FFT of the 10 kHz triangular wave to show a fundamental at 10 kHz and further components at integer multiples of it. The captured spectrum (Fig. 14(a)) shows the fundamental at 10.0 kHz and the next component at 30.1 kHz.


After changing the signal to 20 kHz, the location of the main spectral line changed, as expected (Fig. 14(b)). As expected, the pattern of the harmonics also changed completely when the signal was changed from a triangular wave to a sine wave (Fig. 14(c)).



(a) 10 kHz triangular wave.



(b) 20 kHz triangular wave.

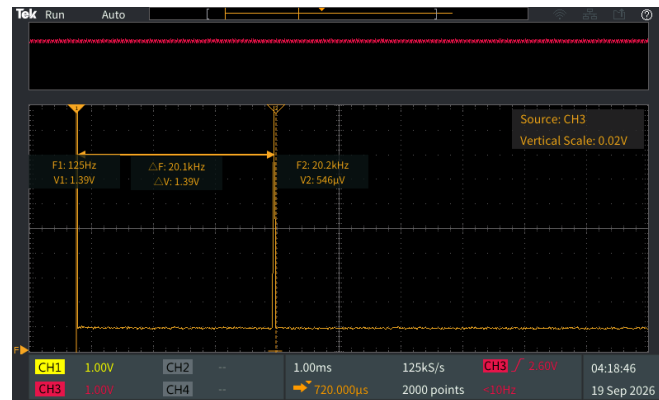

(c) 20 kHz sine wave.

Fig. 14. Time-domain (top) and frequency-domain (bottom) oscilloscope captures.

IV. CONCLUSION

This lab has given the team a better understanding of not only the instrumentation equipment and its calibration, but also of how simulation software processes this information. Spending a lab tinkering with the different oscilloscope functions has also contributed to a better overall understanding of a critical piece of equipment, relevant not only to the course but also to industry.

The biggest takeaways regarding the real-world versus simulation component of the course, in the opinion of this group, concern the Fast Fourier Transform. The team ran up against challenges during the lab with aliasing and with configuring the equipment to view proper waveforms. Encountering the same challenge again in the simulations allowed the group to target its weak points and overcome them. Each member has internalized the Shannon–Nyquist sampling theorem and has a greater understanding of its practical implications.

In simulation Activity 6, the triangle-wave harmonics were found to be very similar to those found in the final experiment of the lab. The team can therefore conclude that all systems are functional and, since the simulation matched reality, that the simulation can be considered a good double check.